

Worksheet 1

Computer Processors (COMP1212)

This worksheet is available in week 1 and will be discussed in week 2's tutorials. You should prepare your solutions to the questions, questions marked with (*) are more difficult and are for discussion in the tutorials.

1. What is the logic circuit symbol used to denote the following gates

- | | |
|---------|----------|
| (a) And | (d) Nand |
| (b) Not | (e) Xor |
| (c) Or | (f) Nor |

2. For each of the following expressions construct:


- a truth table
- a logic circuit diagram
- an equivalent expression in CNF
- an equivalent expression in DNF

- | | |
|---|--|
| (a) $(x \wedge s) \vee (y \wedge \neg s)$ | (d) $(x \vee y) \wedge \neg(x \wedge y)$ |
| (b) $x \wedge \neg s$ | (e) $\neg(x \wedge y)$ |
| (c) $x \wedge s$ | (f) $\neg x \vee y$ |


3. Construct using only nor gates the following gates

- And
- Not
- Nand
- Xor

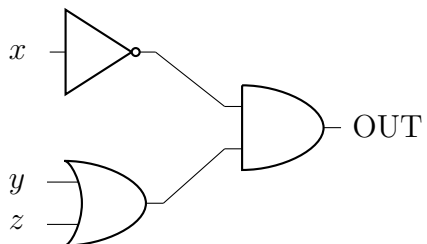
4. Construct boolean expressions which are equivalent to the logic circuits below and draw an equivalent logic circuit that only uses Nand gates.




(a)

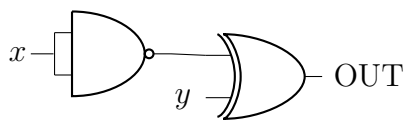

(b)

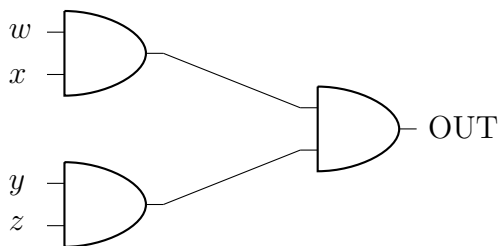

(c)

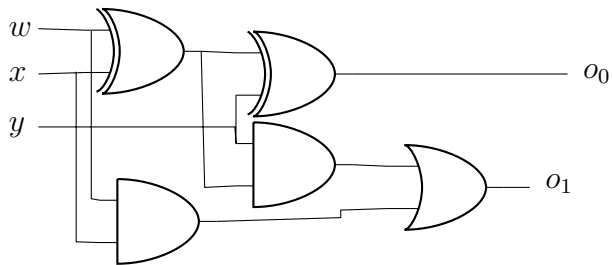

(d)