




UNIVERSITY OF LEEDS

---

# Computer Processors


## Arithmetic Logic Unit

 

Lecture 9

 
# Arithmetic Logic Unit

- The Arithmetic Logic Unit (ALU) is the centerpiece of any modern day computer
- The ALU implements a set of logic commands
- The ALU allows for the selection of which command should be output



 
# Arithmetic Logic Unit

- ALU's implement a fixed set of functions
- Each function can take at most two multi-bit arguments
- The ALU outputs the result of the boolean function and a set of flags


 
# Arithmetic Logic Unit

- The instruction is a set of control bits which select which function the ALU should output
  - And
  - Adder
  - Pre/post processing on inputs/outputs




# Arithmetic Logic Unit

Our specific ALU accepts

- Two 16-bit wide arguments
- A 6-bit wide instruction (control bits)


And outputs

 - A 16-bit wide output
- A bit to indicate if the output is 0
- A bit to indicate if the output is less than 0


 
# Arithmetic Logic Unit

- With a 6-bit wide instruction gives the ALU a possible  $2^6$  (=64) instructions
- We are only interested in 18 of them



# Control bits

- The ALU has the choice between two basic functions logical **And** and **Addition**
- All operations are multi-bit operations
- All of the required components were covered in **Lecture 4 - Common Logic Configurations**

Bit	Description
za	Zero input <b>A</b>
na	Negate input <b>A</b>
zb	Zero input <b>B</b>
nb	Negate input <b>B</b>
f	Select between & and +
no	Negate output

# Control bits

- Each of the 18 configurations of the control bits does something of interest
- Let us consider the control bits set to 001110
  - The ALU is instructed to compute  $a-1$
  - Input **A** is neither zero'ed nor negated
  - Input **B** is zeroed and then negated (2's complement  $-1_{10}$ )
  - f-bit set to **Addition**

za	na	zb	nb	f	no	output
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	$-1$
0	0	1	1	0	0	$a$
1	1	0	0	0	0	$b$
0	0	1	1	0	1	$\neg a$
1	1	0	0	0	1	$\neg b$
0	0	1	1	1	1	$-a$
1	1	0	0	1	1	$-b$
0	1	1	1	1	1	$a + 1$
1	1	0	1	1	1	$b + 1$
0	0	1	1	1	0	$a - 1$
1	1	0	0	1	0	$b - 1$
0	0	0	0	1	0	$a + b$
0	1	0	0	1	1	$a - b$
0	0	0	1	1	1	$b - a$
0	0	0	0	0	0	$a \& b$
0	1	0	1	0	1	$a b$





	za	na	zb	nb	f	no	output
	0	0	1	1	1	0	a-1
a							
b							

	za	na	zb	nb	f	no	output
	0	0	1	1	1	1	-a
a							
b							



	za	na	zb	nb	f	no	output
	0	0	1	1	1	0	a-1
a	a	a	a	a	a-1	a-1	a-1
b	b	b	0	-1 (11111111)			

	za	na	zb	nb	f	no	output
	0	0	1	1	1	1	-a
a	a	a	a	a	a-1	!(a-1)	-a
b	b	b	0	-1			

# Control bits

You should verify that the rest do what is claimed in the table

What do the other 46 control bit configurations do?

za	na	zb	nb	f	no	output
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	$-1$
0	0	1	1	0	0	$a$
1	1	0	0	0	0	$b$
0	0	1	1	0	1	$\neg a$
1	1	0	0	0	1	$\neg b$
0	0	1	1	1	1	$\neg a$
1	1	0	0	1	1	$\neg b$
0	1	1	1	1	1	$a + 1$
1	1	0	1	1	1	$b + 1$
0	0	1	1	1	0	$a - 1$
1	1	0	0	1	0	$b - 1$
0	0	0	0	1	0	$a + b$
0	1	0	0	1	1	$a - b$
0	0	0	1	1	1	$b - a$
0	0	0	0	0	0	$a \& b$
0	1	0	1	0	1	$a   b$

# Implementation

Notice that the ALU is composed of

- A logic circuit that can negate or zero an input (times 2)
- Logic circuits for **Addition** and **And**.
- A logic circuit to select between them
- A logic circuit to negate the output
- A logic circuit to handle flags

*Only the last one has not been implemented already*

- The ALU we implement is quite basic
- No multiplication/division
- No floating point numbers
- No exponentiation (required for some encryptions)
- Modern ALU's support many more operations

***ALU most similar to a  
microprocessor or 1970's ALU's***

# Summary

---

- Introduced the ALU
- Discussed the implementation
- Compared it to current architectures

Interested in logic design? [Digital Logic Design](#)